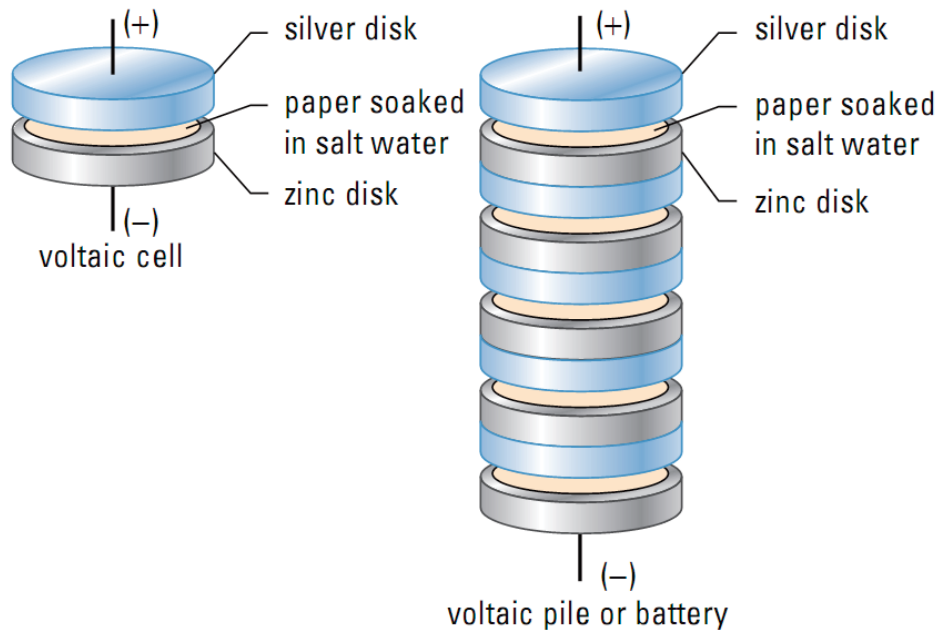


# **Electric Energy, Circuits and Magnetism**

Grade 11 Physics

## **Electricity**

# Electric Potential Difference



# Electric Potential Difference

- ▶ Voltaic Cell:
  - The previous diagram shows a voltaic cell.
  - Voltaic Pile/Battery – a stack of voltaic cell.
- ▶ The anode(+) and cathode(-) sign
  - The anode (upper path)(+)
  - The cathode (lower path)(-)
  - Chose arbitrially

# Electric Potential Difference

- Gravitational Potential*  
*↳ how much energy you carry / kg*  
 *$V = IR$  based on the height*
- ▶ **Electric Potential Difference**
    - The electric potential difference between any two points in a circuit is the quotient of the change in the electric potential energy of charges passing between those points and the quantity of the charge.

*gh* → *Gravitational Potential Difference*  
*↳*

$$V = \frac{\Delta E_Q}{Q}$$

*change in energy*  
*(coulombs) charge*

# Electric Potential Difference

- ▶ **Electric Potential Difference**

$$V = \frac{\Delta E_Q}{Q}$$

Quantity	Symbol	SI unit
electric potential difference	V	V (volt)
change in electrical potential energy	$\Delta E_Q$	J (joule)
quantity of charge	Q	C (coulomb)

## Example Problem

► Q1:

- A battery has a potential difference of 18.0V. How much work is done when a charge of 64.0C moves from the anode to the cathode?

$$V = \frac{\Delta E}{Q}$$

$$\Delta E = VC$$

$$V = 18.0V$$

$$Q = 64.0C$$

## Electric Current

► Electric Current

- Electric current is the quotient of the quantity of charge that moves past a point and the time interval during which the charge is moving.

$$I = \frac{Q}{\Delta t}$$

# Electric Current

## ▶ Electric Current

$$I = \frac{Q}{\Delta t}$$

Quantity	Symbol	SI unit
current	$I$	A (ampere)
amount of charge	$Q$	C (coulomb)
time interval	$\Delta t$	s (second)

## Example Problem

$$I = \frac{Q}{\Delta t}, \quad \Delta t = 2.5 \text{ min} = 150 \text{ sec}$$

### ▶ Q2:

$$V = 120 \text{ V}$$

$$I = 9.60 \text{ A}$$

- The electrical system in your home operates at a potential difference of 120.0volts. A toaster draws 9.60A for a period of 2.50min to toast two slices of bread.
- Find the amount of charge that passed through the toaster.
- Find the amount of energy the toaster converted into heat (and light) while it toasted the bread.

$$\begin{aligned} a) \quad Q &= I \cdot \Delta t \\ &= 9.60 \text{ A} \cdot 150 \text{ sec} \\ &= 1440 \text{ C} \end{aligned}$$

$$b) \quad V = \frac{\Delta E}{Q}$$

$$\begin{aligned} \Delta E &= VQ \\ &= 120 \text{ V} \cdot 1440 \text{ C} \\ &= 172800 \text{ J} \end{aligned}$$

# Charge-Carrying Particles and Elementary Charge ( $e$ )

## ▶ Charge-Carrying Particles

- J.J. Thomson discovered charge-carrying particle in 1897; however people are skeptical about this.

## ▶ Elementary Charge

- Robert Andrews Millikan – Nobel Prize winner in physics in 1923.
- Discovered elementary charge which is the charge of 1 electron or 1 proton.
- Elementary Charge =  $1.602 \times 10^{-19} \text{ C}$

$$\# \text{ of electron} = 1 \text{ C} \Rightarrow \frac{1 \text{ C}}{1.602 \times 10^{-19}} = 6.24 \times 10^{18}$$

# Elementary Charge

## ▶ Elementary Charge

- The amount of charge is the product of the number of elementary charge (electrons or protons) and the magnitude of the elementary charge.

$$Q = Ne$$

# Elementary Charge

## ▶ Elementary Charge

$$1.602 \times 10^{-19}$$

$$Q = Ne$$

constant

Quantity	Symbol	SI unit
amount of charge	$Q$	C (coulomb)
number of elementary charges	$N$	integer (pure number, no unit)
elementary charge	$e$	C (coulomb)

# Resistance of a Conductor

$$V = IR$$

## ▶ Resistance of a Conductor

- The resistance of a conductor is the product of the resistivity and the length divided by the cross-sectional area.

$$R = \rho \frac{L}{A}$$

# Resistance of a Conductor

## ► Resistance of a Conductor

$$R = \rho \frac{L}{A}$$

Quantity	Symbol	SI unit
resistance	$R$	$\Omega$ (ohm)
resistivity	$\rho$	$\Omega \cdot \text{m}$ (ohm metres)
length of conductor	$L$	m (metres)
cross-sectional area	$A$	$\text{m}^2$ (square metres)

# Resistance of a Conductor

## ► Resistance of a Conductor

$$R = \rho \frac{L}{A}$$

Gauge	Diameter (mm)	Resistance ( $\times 10^{-3} \Omega / \text{m}$ )
0	9.35	0.31
10	2.59	2.20
14	1.63	8.54
18	1.02	21.90
22	0.64	51.70

Material	*Resistivity, $\rho$ ( $\Omega \cdot \text{m}$ )
silver	$1.6 \times 10^{-8}$
copper	$1.7 \times 10^{-8}$
aluminum	$2.7 \times 10^{-8}$
tungsten	$5.6 \times 10^{-8}$
Nichrome™	$100 \times 10^{-8}$
carbon	$3500 \times 10^{-8}$
germanium	0.46
glass	$10^{10}$ to $10^{14}$



# Example Problem

► Q4:

- Calculate the resistance of a 15m length of copper wire, at 20°C, that has a diameter of 0.050cm.

$$R = \frac{\rho L}{A}$$

$A_{\text{area}} = \pi R^2$

look up on chart

$$0.00050 \text{ m}$$

## Electric Potential, Current and Resistant

- Electric Potential VS Water Potential
  - Voltage vs Steepness
- Electric Current VS Water Current
  - Charge/Time vs Volume/Time
- Electric Resistant VS Water Resistant
  - Electrical Resistance vs Rocks




# Electric Circuits

## ► Open Circuit


- There is a break in the circuit (perhaps an open switch)

## ► Closed Circuit

- All connections are complete.

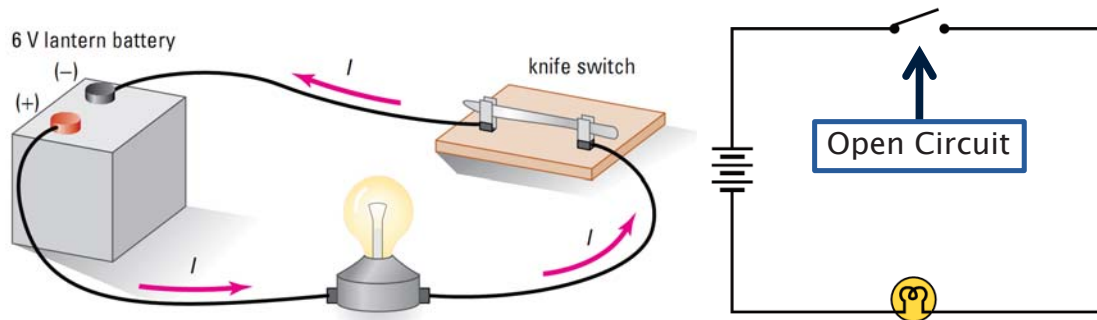
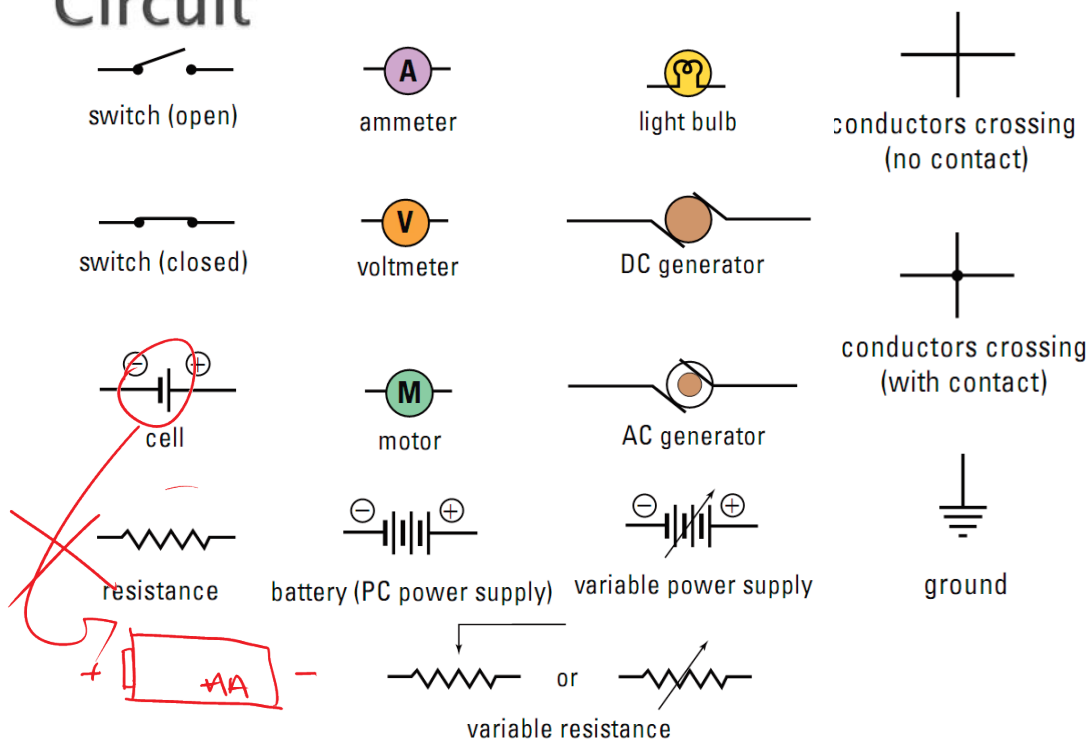
# Symbols for Elements of an Electric Circuit



# Ohm's Law

## ▶ Ohm's Law

- The potential difference across a load equals the product of the current through the load and the resistance of the load.

$$V = IR$$

Quantity	Symbol	SI unit
potential difference	$V$	V (volt)
current	$I$	A (ampere)
resistance	$R$	$\Omega$ (ohm)

## Example Problem

### ▶ Q5:


- What is the resistance of a load if a battery with a 9.0V potential difference causes a current of 0.45A to pass through the load?

$$V = IR$$
$$R = \frac{V}{I}$$

$$V = 9.0 \text{ V}$$
$$I = 0.45 \text{ A}$$

# Series and Parallel Circuits

## Circuit in Series and Parallel

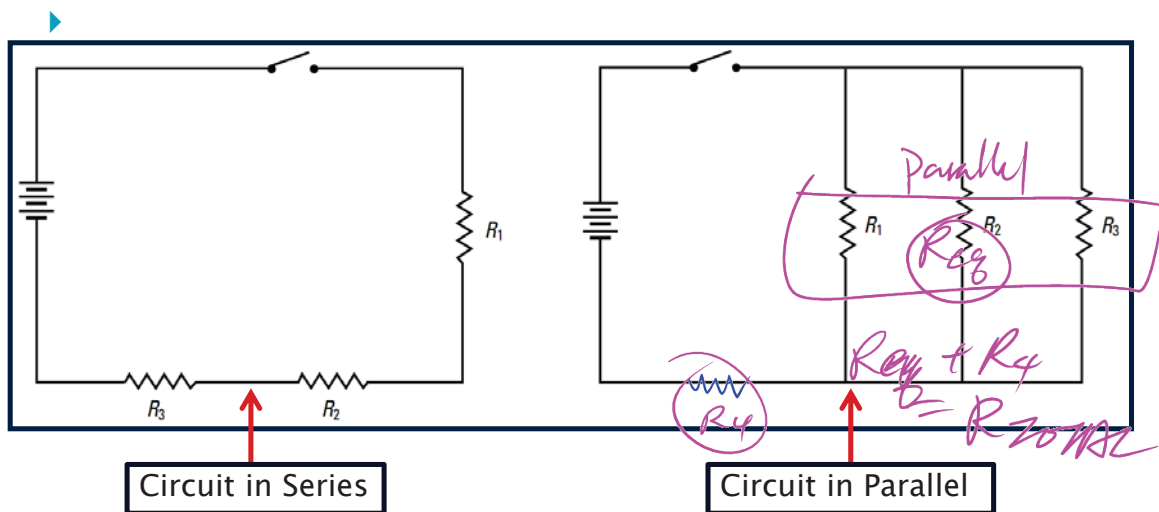

# Circuit in Series

## ► Circuit in Series

- The equivalent resistance of loads in series is the sum of the resistances of the individual loads.

$$R_{eq} = R_1 + R_2 + R_3 + \cdots + R_N$$

Quantity	Symbol	SI unit
equivalent resistance	$R_{eq}$	$\Omega$ (ohm)
resistance of individual loads	$R_{1,2,3,\dots,N}$	$\Omega$ (ohm)

## Example Problem

### ► Q5:


- Four loads ( $3.0\Omega$ ,  $5.0\Omega$ ,  $7.0\Omega$  and  $9.0\Omega$ ) are connected in series to a  $12V$  battery. Find
  - The equivalent resistance of the circuit
  - The total current in the circuit
  - The potential difference across the  $7.0\Omega$  load

$$R_{eq} = 3 + 5 + 7 + 9 = 24\Omega$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{12}{24} = 0.5A$$

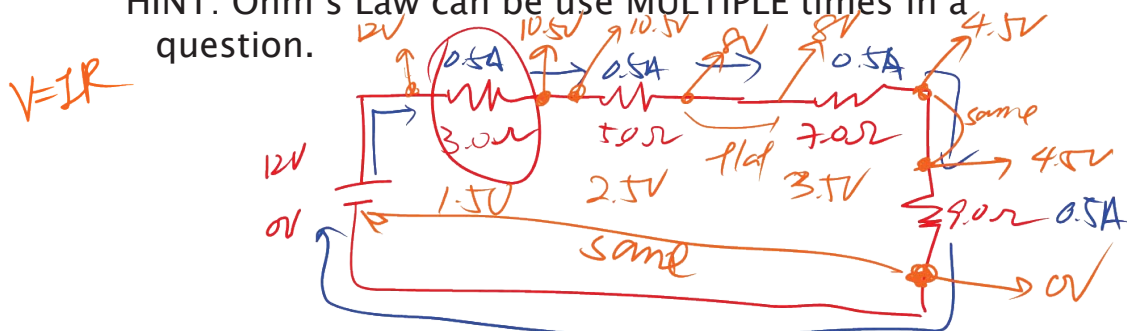HINT: Ohm's Law can be use MULTIPLE times in a question.



# Circuit in Parallel

## ► Circuit in Parallel

- The inverse of the equivalent resistance for resistors connected in parallel is the sum of the inverses of the individual resistances.


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$$

Quantity	Symbol	SI unit
equivalent resistance	$R_{eq}$	$\Omega$ (ohm)
resistance of the individual loads	$R_1, R_2, R_3, \dots, R_N$	$\Omega$ (ohm)

## Example Problem
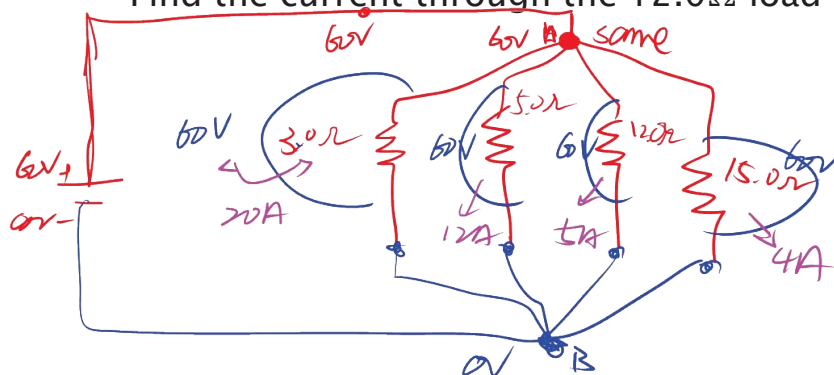
### ► Q6


- A 60V battery is connected to four loads of  $3.0\Omega$ ,  $5.0\Omega$ ,  $12.0\Omega$  and  $15.0\Omega$  in parallel.
  - Find the equivalent resistance of the four combined loads
  - Find the total current leaving the battery →
  - Find the current through the  $12.0\Omega$  load



## Example Problem
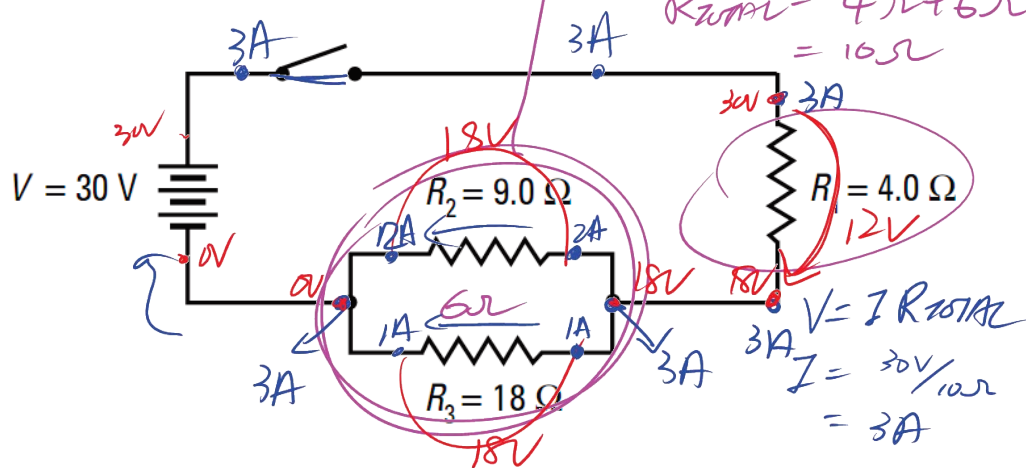
### ► Q7:

- Find the equivalent resistance of the entire circuit shown in the diagram, as well as the current through, and the potential difference across, each load.



## Internal Resistance, Electromotive Force, Terminal Voltage

### ► Internal Resistance

- Referring to the resistance within the battery itself
- Like an engine itself would create friction inside. The engine needs to at least overcome the friction in itself.
- Same as battery

### ► Electromotive Force (*emf* or $\mathcal{E}$ )

- With out internal resistance
  - terminal voltage =  $\mathcal{E}$

# Terminal Voltage and *emf*

- ▶ Terminal Voltage and *emf*
  - The terminal voltage (or potential difference across the poles) of a battery is the difference of the *emf*( $\mathcal{E}$ ) of the battery and the potential drop across the internal resistance of the battery.

$$V_S = \mathcal{E} - V_{\text{int}}$$

# Terminal Voltage and *emf*

- ▶ Terminal Voltage and *emf*

$$V_S = \mathcal{E} - V_{\text{int}}$$

If not current is passing through a battery, then the potential difference across the internal resistance will be zero ( $V_{\text{int}}=0$ )

Quantity	Symbol	SI unit
terminal voltage	$V_S$	V (volt)
electromotive force	$\mathcal{E}$	V (volt)
internal potential drop of a battery	$V_{\text{int}}$	V (volt)



## Example Problem

- ▶ Q8:
  - A battery with an *emf* of 9.0V has an internal resistance of  $0.0500\Omega$ . Calculate the potential difference lost to the internal resistance, and the terminal voltage of the battery, if it is connected to an external resistance of  $4.00\Omega$ .

## Electric Power

- ▶ Electric Power
  - Power is the product of current and potential difference.

$$P = IV$$

Quantity	Symbol	SI unit
power	$P$	W (watt)
current	$I$	A (ampere)
potential difference	$V$	V (volt)

# Example Problem

- ▶ Q9:
  - What is the power rating of a segment of Nichrome wire that draws a current of 2.5A when connected to a 12V battery?

## Power and Voltage

- ▶ Power and Voltage
  - Most of electronic appliance indicates the power used and required voltage
  - Fried appliances when travelling

# Example Problem

► Q10:

- In North America, the standard electric outlet has a potential difference of 120V. In Europe, it is 240V. How does the dissimilarity in potential difference affect power output? What would be the power output of a 100W–120V light bulb if it was connected to a 240V system?

## Alternative Equations for Power

► Alternative Equations for Power

$$P = \frac{V^2}{R}$$

$$P = I^2 R$$

Quantity	Symbol	SI unit
power	$P$	W (watt)
potential difference	$V$	V (volt)
resistance	$R$	$\Omega$ (ohm)
current	$I$	A (ampere)

## Example Problem

### ► Q11:

- An electric kettle is rated at 1500W for a 120V potential difference.
  - What is the resistance of the heating element of the kettle?
  - What will be the power output if the potential difference falls to 108V?

## Example Problem

### ► Q12:

- A family has its television set on for an average 4.0h per day. If the television set is rated at 80W and energy costs \$0.070 per kWh, how much would it cost to operate the set for 30 days?

# Magnetism

## Magnetism

### ► Magnetism

- The magnitude of the force is proportional to the inverse of the square of the distance.

$$|\vec{F}| \propto \frac{1}{d^2}$$

### **RULES FOR MAGNETIC INTERACTIONS**


1. Like poles repel each other.
2. Unlike poles attract each other.
3. The force of attraction varies inversely as the square of the distance between the poles.

# Electricity and Magnetism


## Right-hand Rule #1

- ▶ Right-hand Rule #1

- Current Induced Magnetic Field

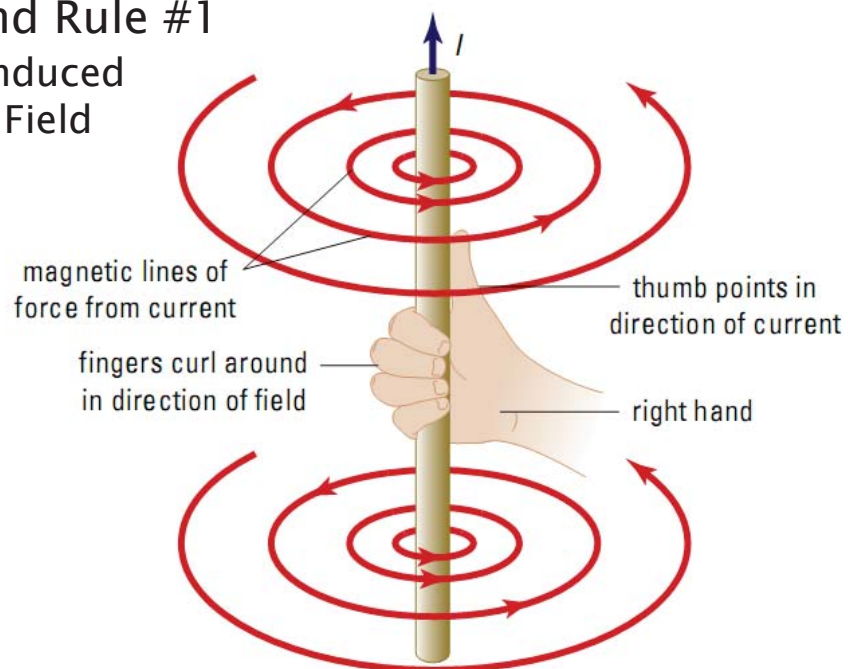


# Right-hand Rule #1

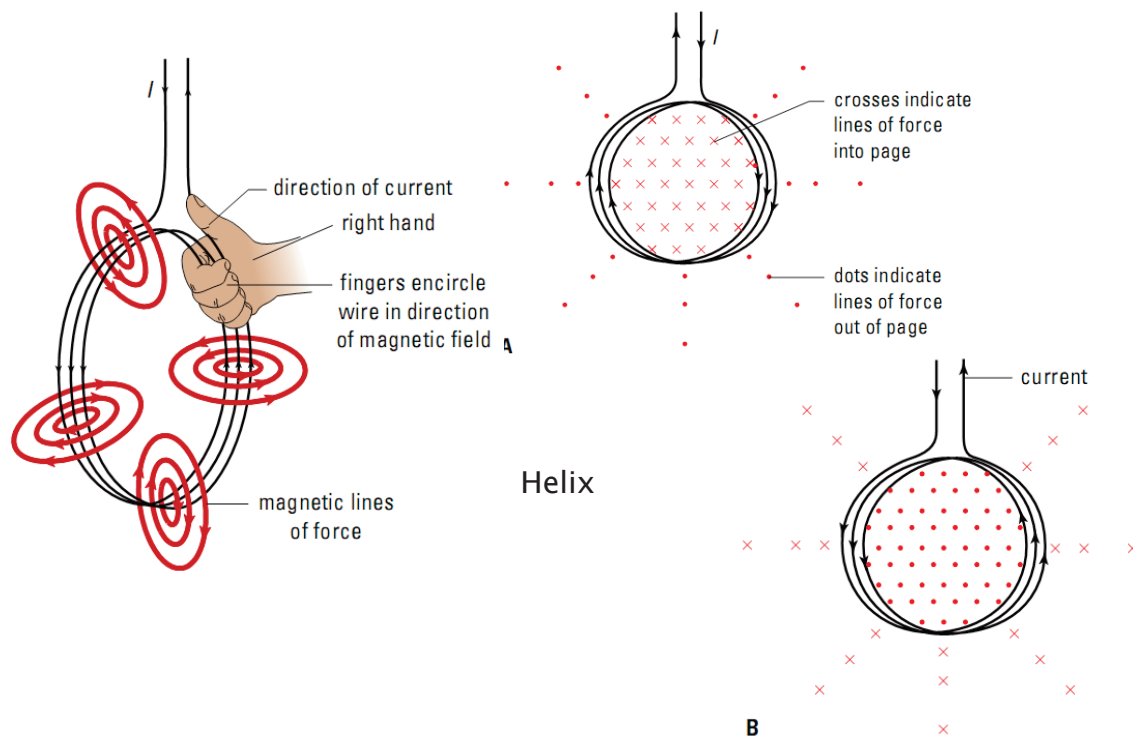

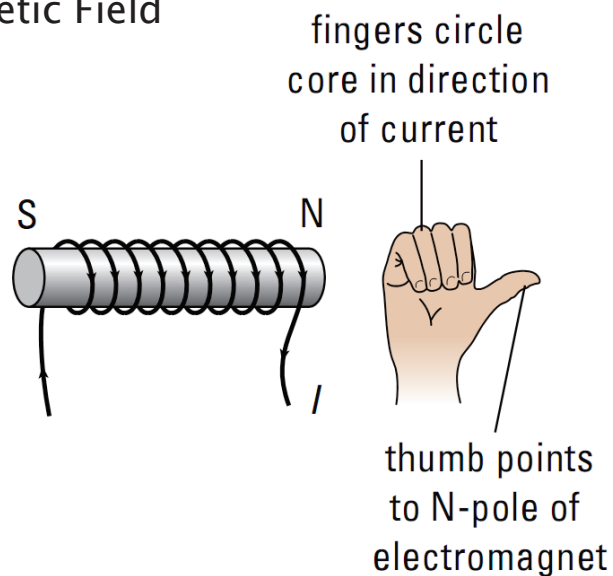
# Right-hand Rule #2

- ▶ Right-hand Rule #2
  - Poles of the Magnetic Field


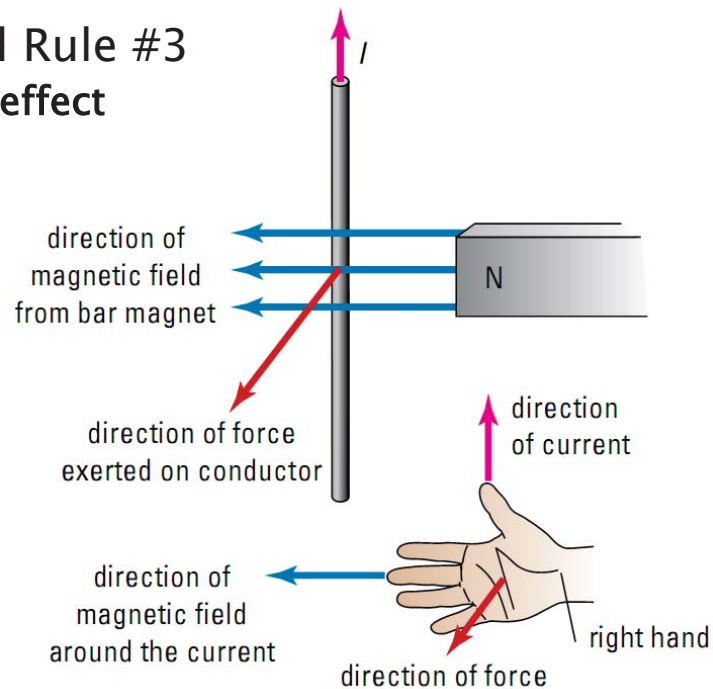
## Right-hand Rule #3

- ▶ Right-hand Rule #3
  - The motor effect



## Magnetic Field Strength and Magnetic Force

- ▶ Magnetic Field Strength and Magnetic Force
  - The magnetic field strength perpendicular to the conductor is the quotient of the magnetic force and the current and length of the conductor.

$$B_{\perp} = \frac{F}{IL}$$

$$L = n\ell$$



# Magnetic Field Strength and Magnetic Force

## ► Magnetic Field Strength and Motor Force

$$B_{\perp} = \frac{F}{IL}$$

$$L = n\ell$$

Quantity	Symbol	SI unit
magnetic field strength	$B$	tesla (T)
“perpendicular to”	$\perp$	
motor force	$F$	newton (N)
current	$I$	amp (A)
length of conductor	$L$	metre (m)
number of coil turns	$n$	no unit
length of each turn	$\ell$	metre (m)


## Example Problem

- Q1:
  - A length of straight conductor carries a current of 4.8A into page at right angles to a magnetic field. The length of the conductor that lies inside the magnetic field is 25cm (0.25m). If this conductor experiences a force of 0.60N to the right, what is the magnetic field strength acting on the current?

# DC Motor
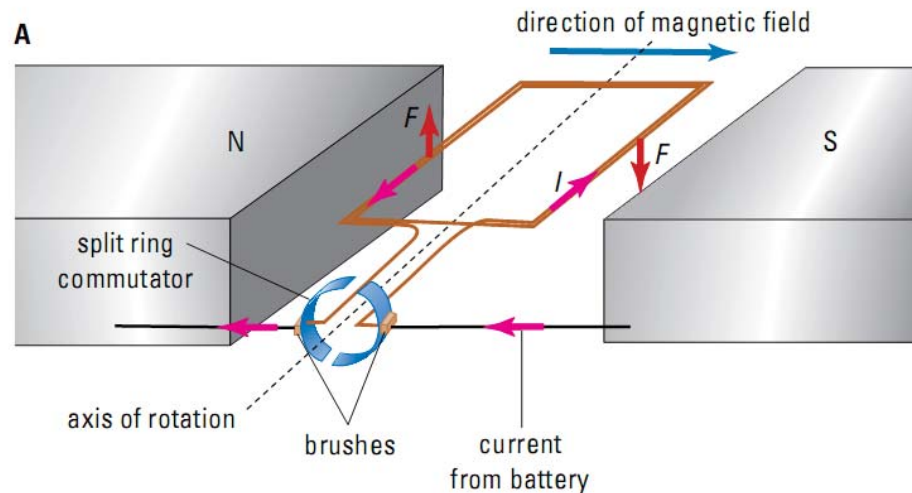
## ▶ DC Motor


- The direction of the magnetic pole is important



# DC Motor
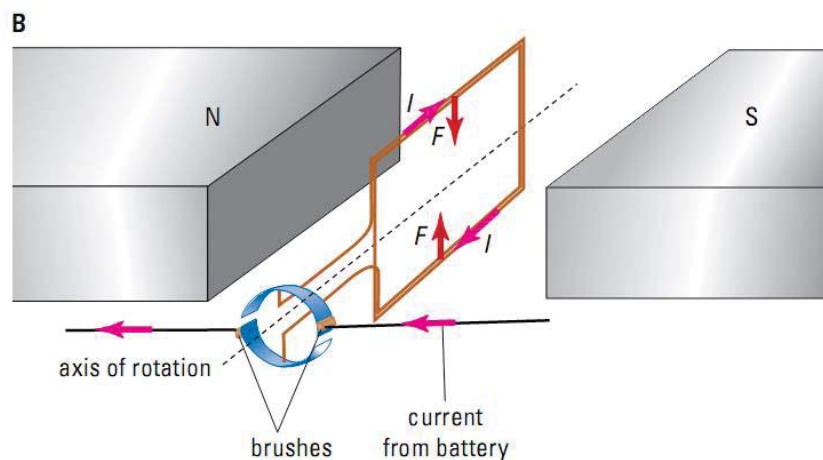
## ▶ DC Motor

- The direction of the magnetic pole is important
- Notice that the direction of the current is changed
- A different magnetic pole.



# Electromagnetic Induction


## Electromagnetic Induction

- ▶ Electromagnetic Induction
  - Current induces changing magnetic field strength
  - Does changing magnetic field strength induces current?
  - DOES IT????? Or DOES IT NOT???????

# Right-hand Rules #4

## ▶ Right-hand Rules #4


- The **generator effect**

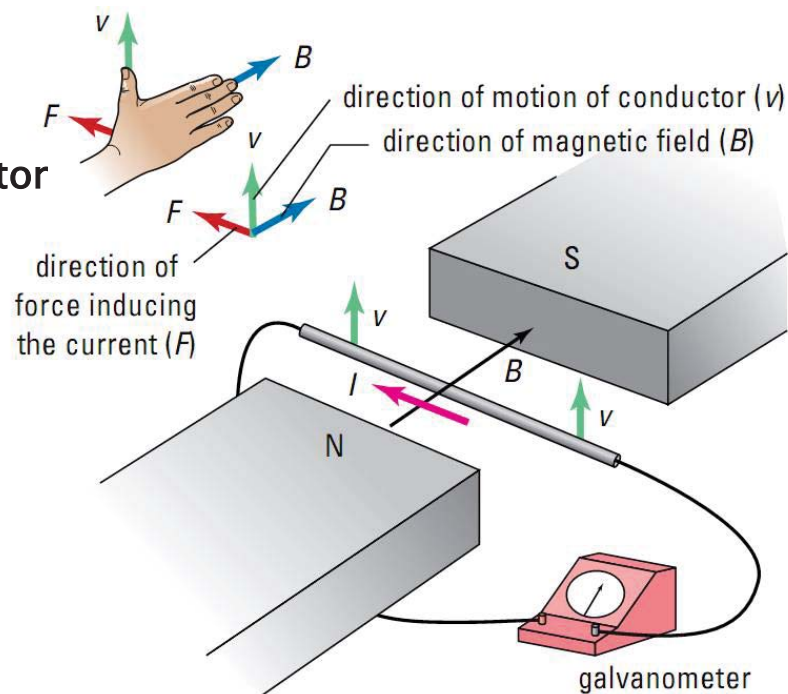

# Right-hand Rules #4


## ▶ Right-hand Rules #4

- The **generator effect**

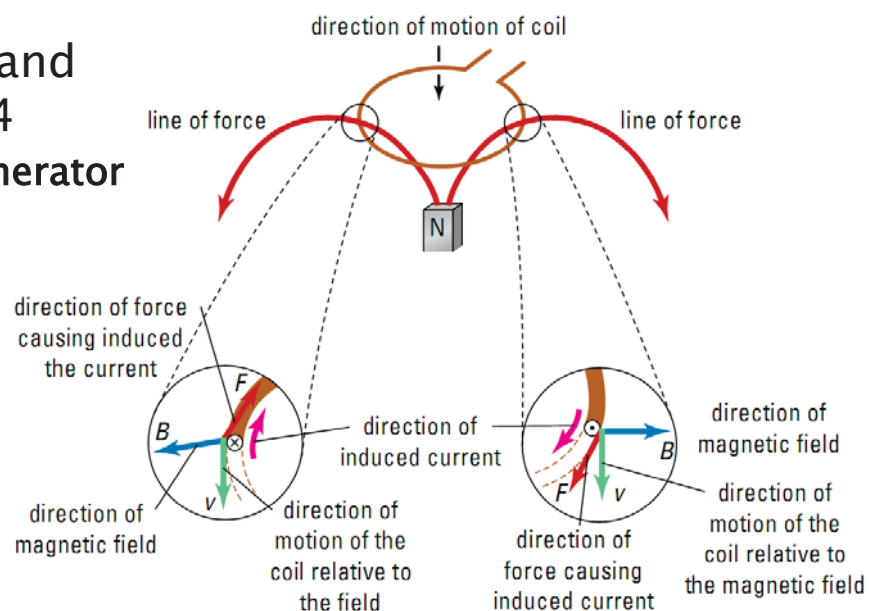
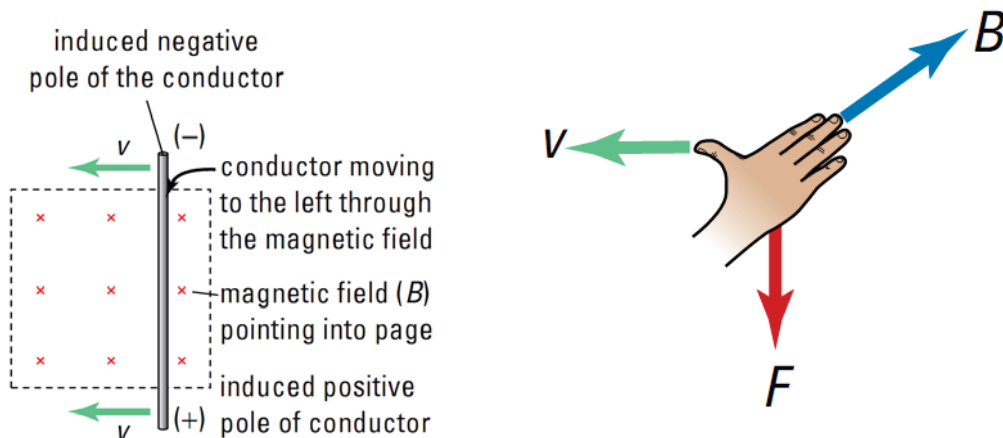
# Conductor through Magnetic Field

- ▶ Conductor through Magnetic Field
  - Causes the conductor to have a polarity difference in charges similar to a battery.



## Lenz's Law

- ▶ Lenz's Law
  - When a conductor interacts with a magnetic field, there must be an induced current that opposes the interaction, because of the law of conservation of energy.
  - Video!

